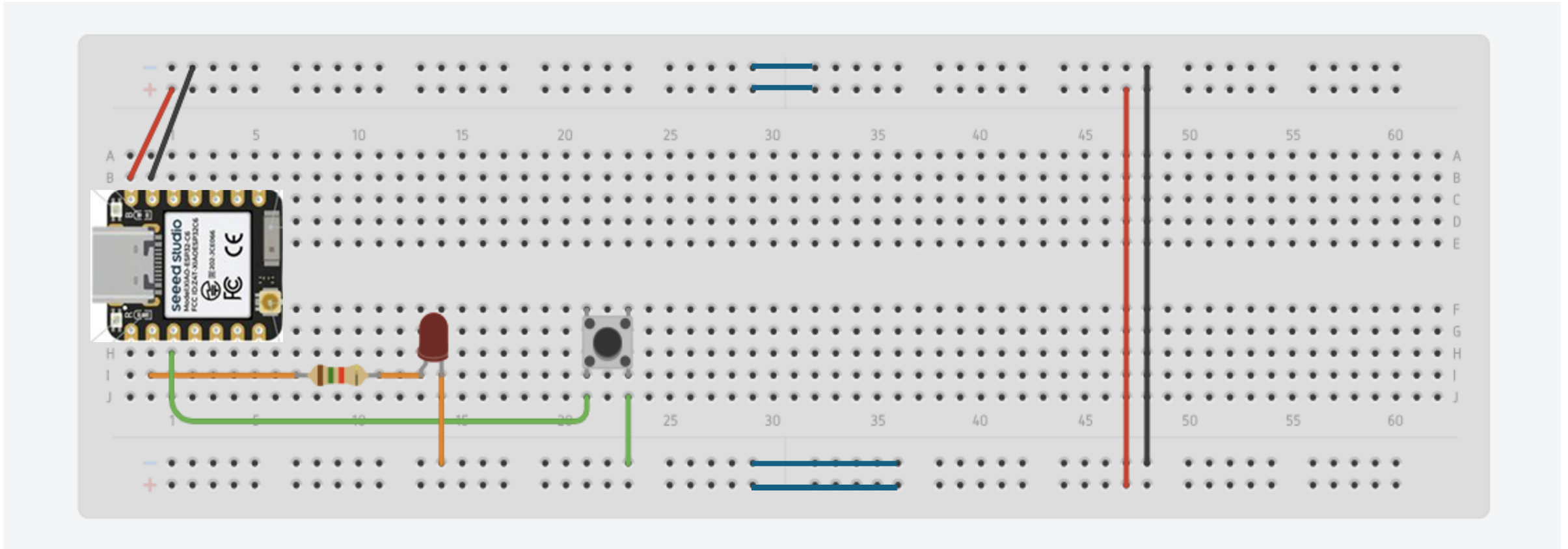


A circuit where an LED lights up when you press a button




- The shorter pin of the LED connects to GND.

Pictorial circuit diagram tool “Tinkercad”
<https://www.tinkercad.com/dashboard>



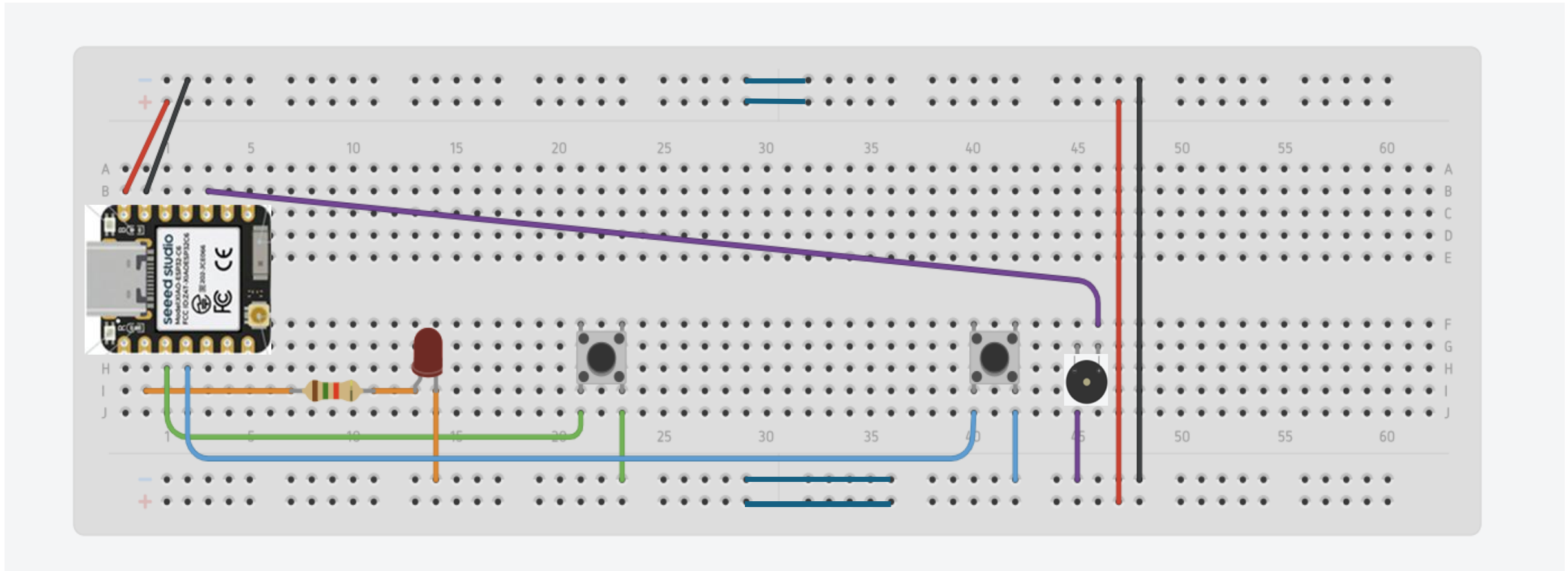
A circuit where a buzzer sounds when you press a button



- The side of the buzzer marked with “+” is the positive terminal.



A circuit with a display

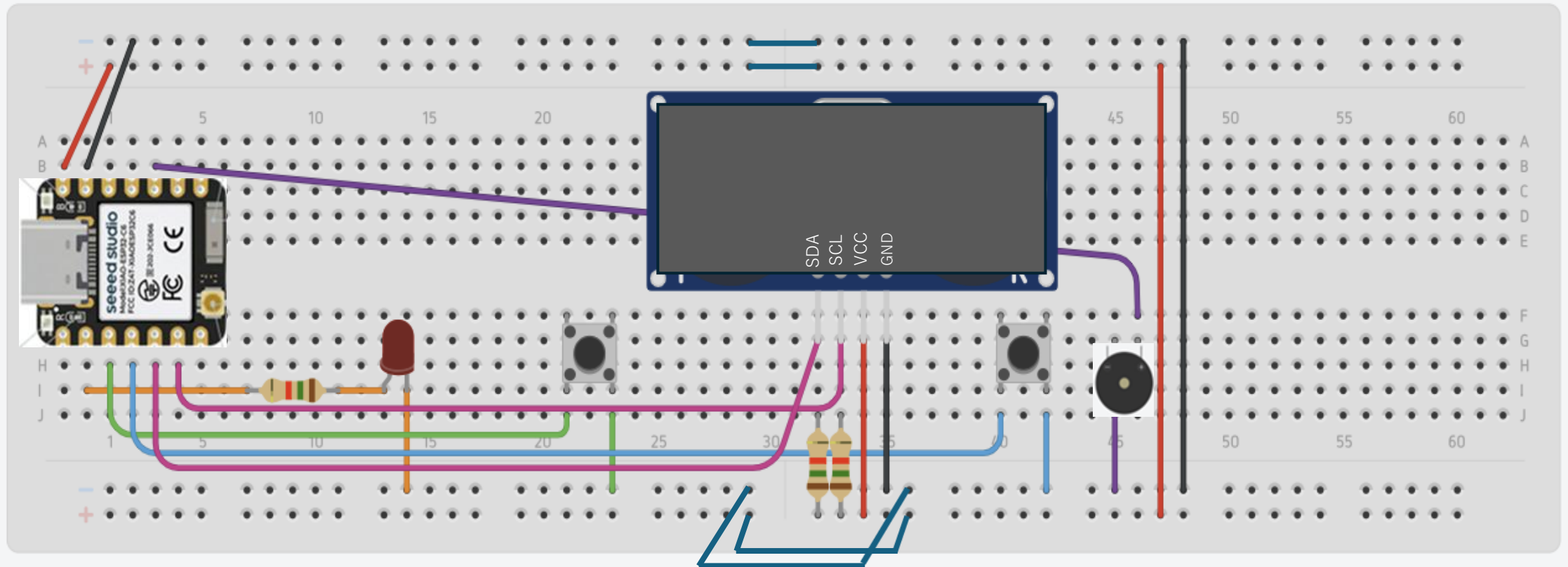

A circuit with a temperature sensor

